

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ



شبكة المعلومات الجامعية التوثيق الالكتروني والميكروفيلم



شبكة المعلومات الجامعية

جامعة عين شمس

التوثيق الالكتروني والميكروفيلم

قسم

نقسم بالله العظيم أن المادة التي تم توثيقها وتسجيلها
على هذه الأفلام قد أعدت دون أية تغيرات



يجب أن

تحفظ هذه الأفلام بعيدا عن الغبار

في درجة حرارة من ١٥-٢٥ مئوية ورطوبة نسبية من ٢٠-٤٠%

To be Kept away from Dust in Dry Cool place of
15-25- c and relative humidity 20-40%

بعض الوثائق الاصليّة تالفه

بالرسالة صفحات
لم ترد بالأصل

**CONTROLLING FREQUENCY OF
SELF-EXCITED INDUCTION GENERATOR
USED IN AUTONOMOUS WIND-TURBINES
BY MEANS OF
TERMINAL-EXCITATION CAPACITANCE.**

By

Abdul-Mateen H. Hameed

B.Sc. Electrical Power and Machines Engineering

A Thesis Presented to the Faculty of Engineering
of Cairo University
in Partial Fulfillment of the Requirements for the Degree of
Master of Science
in Electrical Power and Machines Engineering

Faculty of Engineering
Cairo University
Egypt
December -2007

11/2/07

**CONTROLLING FREQUENCY OF
SELF-EXCITED INDUCTION GENERATOR
USED IN AUTONOMOUS WIND-TURBINES
BY MEANS OF
TERMINAL-EXCITATION CAPACITANCE**

By

Abdul-Mateen H. Hameed

B.Sc. Electrical Power and Machines Engineering

A Thesis Presented to the Faculty of Engineering
of Cairo University
in Partial Fulfillment of the Requirements for the Degree of
Master of Science
in Electrical Power and Machines Engineering

Under the Supervision of

Prof. Dr. Mohamed M. Abdel Aziz
Electric Power and machine Department
Faculty of Engineering-Cairo University

Prof. Dr. Adel. A. Shaltout
Electric Power and machine Department
Faculty of Engineering-Cairo University

Faculty of Engineering
Cairo University
Egypt
December -2007

11
32

**CONTROLLING FREQUENCY OF
SELF-EXCITED INDUCTION GENERATOR
USED IN AUTONOMOUS WIND-TURBINES
BY MEANS OF
TERMINAL-EXCITATION CAPACITANCE**

By

Abdul-Mateen H. Hameed


B.Sc. Electrical Power and Machines Engineering

A Thesis Presented to the Faculty of Engineering
of Cairo University
in Partial Fulfillment of the Requirements for the Degree of
Master of Science
in Electrical Power and Machines Engineering

H.T. Darreh

Approved by the Examining Committee

Prof. Dr. Mohamed M. Abdel Aziz

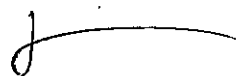

Advisor


Prof. Dr. Adel A. Shaltout



Advisor

Pro. Dr. Essam El-Deen M. Abou Elzahab

Faculty of Engineering-Cairo University

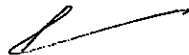

Member

Pro. Dr. Mohsen Taha Elhagri
National Research Center



Member

Faculty of Engineering
Cairo University
Egypt
December -2007

Table of Contents

Table of Contents	ii
List of Tables	v
List of Figures	vi
List of Symbols	x
Acknowledgments	xi
ABSTRACT.....	xii
 1 Introduction	 1
1.1 Background information.....	1
1.2 Classification of Wind Energy Systems.....	4
1.2.1 Constant-Speed Constant-Frequency.....	4
1.2.2 Variable-Speed Variable-Frequency.....	5
1.2.3 Variable-speed Constant-frequency.....	5
1.2.3.1 AC-DC-AC Link.....	5
1.2.3.2 Variable Terminal Capacitor Banks.....	7
 2 Analytical Study	 9
2.1 Introduction.....	9
2.2 Equivalent Circuit Model of Induction Machines.....	10
2.2.1 Approximate Equivalent Circuit.....	10
2.2.2 IEEE Recommended Equivalent Circuit	11
2.3 The Practical Equivalent Circuit of Isolated SEIG at No-Load.....	12
2.4 The Magnetizing Curve of The test Machine.....	14
2.5 The Critical Values of Excitation Capacitance.....	15
2.6 The Effect of Rotor Speed on the Frequency.....	25
2.6.1 At No-Load.....	25
2.6.2 Under Resistive Load.....	31
2.6.3 Under Inductive Load.....	41
2.6.4 Under Capacitive Load.....	49
2.7 The Effect of Excitation-Capacitance on the Frequency.....	57
2.7.1 At No-Load.....	57
2.7.2 Under Resistive Load.....	61
2.7.3 Under Inductive Load	67
2.7.4 Under Capacitive Load	74

3 Stabilizing Frequency by means of Terminal Excitation-Capacitance.....	80
3.1 Introduction.....	80
3.2 Stabilizing Frequency At No-Load.....	81
3.3 Stabilizing Frequency under Resistive Load.....	84
3.4 Stabilizing Frequency under Inductive Load.....	91
3.5 Stabilizing Frequency under Capacitive Load.....	98
4 Application and Experimental Work.....	106
4.1 Static Var Compensator.....	106
4.1.1 Fixed Capacitor, Thyristor-Controlled Reactor (FC-TCR).....	107
4.1.2 Thyristor-Switched Capacitor (TSC)	109
4.1.3 Thyristor-Controlled Reactor, Thyristor-Switched Capacitor (TCR-TSC)	110
4.2 Open Loop Control System.....	111
4.2.1 Zero crossing detector (ZCD)	114
4.2.2 Ramp generator circuit.....	115
4.2.3 Level detector.....	116
4.2.4 Differentiator and pulse isolation.....	117
4.2.4.1 Opto-isolator (thyristor-triac-thyristor)	118
4.2.4.2 Pulse transformer.....	118
4.3 Closed Loop Control System.....	119
4.4 Experimental Work	123
4.4.1 Experimental work description.....	123
4.4.2 Experimental work steps.....	125
4.4.3 Different types of connection.....	127
5 Problem Simulation	128
5.1 Introduction.....	128
5.2 Wind Turbine Model.....	129
5.3 Induction (Asynchronous) Generator Model.....	131
5.4 Self-Excitation and Closed-Loop Control System.....	134
5.5 Overall System Operation.....	134
6 Summary and Future Work.....	139
6.1 Summary.....	139
6.2 Conclusion.....	141
7 References	142

8 Appendices.....	146
8.1. The effect of frequency variations.....	146
8.1.1. The effect of frequency variations on induction motor.....	146
8.1.2. The effect of frequency variations on water pump.....	148
8.1.3. The effect of frequency variations on refrigerator.....	149
8.1.4. The effect of frequency variations on microwave oven.....	151
8.1.5. The effect of frequency variations on transformer.....	155
8.1.6. The effect of frequency variations on transmission lines.....	157
8.1.7. The effect of frequency variations on electronic equipment.....	158
8.2. Magnetizing Curve of the Machine.....	159
8.3. Estimating the Equivalent Circuit Parameters: DC-Test, No-Load Test, and Blocked-Rotor Test.....	160
8.4. Comparing the initial costs of solar and wind energy.....	163
8.5. Table Appendix.....	164
 9 Arabic Title Page & Arabic Abstract.....	

List of Tables

- Table 4-1: Experimental measurements.....125
- Table 4-2: Experimental measurements at different types of connection.....127
- Table 5-1: The output signals of Induction generator block133
- Table (8-1) : General Effect of Frequency and Voltage Variation on Induction Motor Characteristics.....147
- Table (8-2): Values of Measured Voltages and Current for Magnetizing Curve....164

List of Figures

No.	Title	Page No.
1.1	Simplified Diagram of AC-Dc-Ac Link	6
1.2	Circuit Currents [a]: Ac Current with Variable Frequency [b]: Dc Current [c]: Ac Current with Constant Frequency	6
1.3	Simplified Figure of SVC	9
2.1	Equivalent Circuit model of Induction Machine	10
2.1.a	Approximate Equivalent Circuit	10
2.1.b	Approximate Equivalent Circuit with Omitted Resistance R_c	11
2.1.c	IEEE-Recommended Equivalent Circuit	12
2.2	No-Load Equivalent Circuit of Induction Generator with Excitation Capacitance	12
2.3	Practical No-Load Equivalent Circuit of Induction Generator with Excitation Capacitance	12
2.3.a	Practical No-Load Equivalent Circuit of Self-Excited Induction Generator at No-Load	14
2.3.b	Practical No-Load Equivalent Circuit of Self-Excited Induction Generator	14
2.4	The Magnetizing Curve	15
2.3.b.re	Practical No-Load Equivalent Circuit of Self-Excited Induction Generator	16
2.5	Critical Values of Frequency in order to Sustain Self-Excitation	19
2.6	Critical Values of Terminal Capacitance In order to Sustain Self-Excitation	20
2.7	Minimum Values of Terminal Capacitance In order to Sustain Self-Excitation	21
2.8	Equivalent Circuit of Self-Excited Induction Generator	22
2.9	Terminal Voltages That Meet Self-Excitation Area	23
2.10	Circuit Current That Meet Self-Excitation Area	24
2.11	Variation of f versus n at Constant C under No-Load	26
2.12	Variation of X_m versus n at constant C under No-Load	27
2.13	Variation of V_g versus n at constant C under No-Load	28
2.14.a	Variation of I_s versus n at constant C under No-Load	29
2.14.b	Variation of I_L versus n at constant C under No-Load	30
2.15	Variation of V_t versus n at constant C under No-Load	31
2.16.a	Equivalent circuit of self excited induction generator under resistive load	31
2.16.b	Variation of f versus n at constant C under Resistive Load	33
2.17	Variation of X_m versus n at constant C under Resistive Load	34
2.18	Variation of V_g versus n at constant C under Resistive Load	35
2.19	Variation of V_t versus n at constant C under Resistive Load	36
2.20	Variation of I_s versus n at constant C under Resistive Load	37
2.21	Variation of I_L versus n at constant C under Resistive Load	38
2.22	Variation of P_{loss} versus n at constant C under Resistive Load	39
2.23.a	Variation of P_{in} versus n at constant C under Resistive Load	39
2.23.b	Variation of Output Power P_{out} versus n at constant C under Resistive Load	40
2.24	Variation of Efficiency η versus n at constant C under Resistive Load	41
2.25.a	Equivalent circuit of self excited induction generator under inductive load	41

2.25	Variation of f versus n at constant C under Inductive Load	43
2.26	Variation of X_m versus n at constant C under Inductive Load	44
2.27	Variation of V_g versus n at constant C under Inductive Load	45
2.28	Variation of V_t versus n at constant C under Inductive Load	45
2.29	Variation of I_s versus n at constant C under Inductive Load	46
2.30	Variation of I_L versus n at constant C under Inductive Load	47
2.31	Variation of P_{in} versus n at constant C under Inductive Load	48
2.32	Variation of P_{Loss} versus n at constant C under Inductive Load	48
2.33	Variation of Efficiency η versus n at Constant C under Inductive Load	49
2.34.a	Equivalent circuit of self excited induction generator under capacitive load	49
2.34	Variation of f versus n at constant C under Capacitive Load	51
2.35	Variation of X_m versus n at constant C under Capacitive Load	52
2.36	Variation of V_g versus n at constant C under Capacitive Load	53
2.37	Variation of V_t versus n at constant C under Capacitive Load	53
2.38	Variation of I versus n at constant C under Capacitive Load	54
2.39	Variation of I_L versus n at constant C under Capacitive Load	55
2.40	Variation of P_{in} versus n at constant C under Capacitive Load	55
2.41	Variation of P_{Loss} versus n at constant C under Capacitive Load	56
2.42	Variation of Efficiency η versus n at Constant C under Capacitive Load	56
2.43	Variation of f versus C at constant n under No-Load	57
2.44	Variation of X_m versus C at constant n under No-Load	58
2.45	Variation of V_g versus C at constant n under No-Load	59
2.46	Variation of I versus C at constant n under No-Load	60
2.47	Variation of V_t versus C at constant n under No-Load	60
2.48	Variation of f versus C under Resistive Load	61
2.49	Variation of X_m versus C under Resistive Load	62
2.50	Variation of V_g versus C under Resistive Load	63
2.51	Variation of V_t versus C under Resistive Load	64
2.52	Variation of I_s versus C under Resistive Load	65
2.53	Variation of I_L versus C under Resistive Load	65
2.54	Variations of P_{in} versus C under Resistive Load	66
2.55	Variations of P_{out} versus C under Resistive Load	66
2.56	Variation of Efficiency η versus C under Resistive Load	67
2.57	Variation of f versus C Under Inductive Load	68
2.58	Variation of X_m versus C Under Inductive Load	69
2.59	Variation of V_g versus C Under Inductive Load	69
2.60	Variation of V_t versus C Under Inductive Load	70
2.61	Variation of I_s versus C Under Inductive Load	71
2.62	Variation of I_L versus C Under Inductive Load	71
2.63	Variation of P_{in} versus C Under Inductive Load	72
2.64	Variation of P_{loss} versus C under Inductive Load	73
2.65	Variation of Efficiency versus C at Constant n Under Inductive Load	73
2.66	Variation of f versus C at Constant n under Capacitive Load	74
2.67	Variation of X_m versus C at Constant n under Capacitive Load	75

2.68	Variation of V_g versus C at Constant n under Capacitive Load	76
2.69	Variation of V_t versus C at Constant n under Capacitive Load	76
2.70	Variation of I_s versus C at Constant n under Capacitive Load	77
2.71	Variation of I_L versus C at Constant n under Capacitive Load	77
2.72	Variation of P_{in} versus C at Constant n under Capacitive Load	78
2.73	Variation of P_{out} versus C at Constant n under Capacitive Load	78
2.74	Variation of Efficiency η versus C at Constant n Under Capacitive Load	79
3.1	Variation of C versus n in order to maintain $f=1$ p.u under No- Load	81
3.2	Variation of X_m versus n in order to maintain $f=1$ p.u under No- Load	82
3.3	Variation of Voltages versus n in order to maintain $f=1$ p.u under No- Load	83
3.4	Variation of Currents n at constant frequency $f=1$ p.u under No- Load	84
3.5	Variation of C versus n in order to maintain $f=1$ p.u under resistive Load	85
3.6	Variation of the required KVA versus n to maintain $f=1$ p.u under resistive Load	86
3.7	Variation of X_m versus n in order to maintain $f=1$ p.u under resistive Load	86
3.8	Variation of V_g versus n in order to maintain $f=1$ p.u under resistive Load	87
3.9	Variation of V_t versus n in order to maintain $f=1$ p.u under resistive Load	87
3.10	Variation of I_s versus n in order to maintain $f=1$ p.u under resistive Load	88
3.11	Variation of I_L versus n in order to maintain $f=1$ p.u under resistive Load	89
3.12	Variation of P_{in} versus n in order to maintain $f=1$ p.u under resistive Load	90
3.13	Variation of P_{Loss} versus n in order to maintain $f=1$ p.u under resistive Load	90
3.14	Variation of Efficiency η versus n in order to maintain $f=1$ p.u under resistive Load	91
3.15	Variation of C versus n in order to maintain $f=1$ p.u under inductive Load	92
3.16	Variation of the required KVA versus n in order to maintain $f=1$ p.u under inductive Load	93
3.17	Variation of X_m versus n in order to maintain $f=1$ p.u under inductive Load	93
3.18	Variation of V_g versus n in order to maintain $f=1$ p.u under inductive Load	94
3.19	Variation of V_t versus n in order to maintain $f=1$ p.u under inductive Load	95
3.20	Variation of I_s versus n in order to maintain $f=1$ p.u under inductive Load	95
3.21	Variation of I_L versus n in order to maintain $f=1$ p.u under inductive Load	96
3.22	Variation of P_{in} versus n in order to maintain $f=1$ p.u under inductive Load	97
3.23	Variation of P_{loss} versus n in order to maintain $f=1$ p.u under inductive Load	97
3.24	Variation of Efficiency η versus n in order to maintain $f=1$ p.u under inductive Load	98
3.25	Variation of Terminal Capacitance C versus n to maintain $f=1$ p.u under Capacitive Load	99
3.26	Variation of the required KVA versus n in order to maintain $f=1$ p.u under Capacitive Load	100
3.27	Variation of X_m versus n to maintain $f=1$ p.u under Capacitive Load	100
3.28	Variation of V_g versus n to maintain $f=1$ p.u under Capacitive Load	101
3.29	Variation of V_t versus n to maintain $f=1$ p.u under Capacitive Load	102
3.30	Variation of I_s versus n to maintain $f=1$ p.u under Capacitive Load	102
3.31	Variation of I_L versus n to maintain $f=1$ p.u under Capacitive Load	103
3.32	Variation of P_{in} versus n to maintain $f=1$ p.u under Capacitive Load	104
3.33	Variation of P_{loss} versus n to maintain $f=1$ p.u under Capacitive Load	104
3.34	Variation of Efficiency η versus n to maintain $f=1$ p.u under Capacitive Load	105
4.1.a	Per Phase Diagram of FC-TCR Static Var Compensator	107
4.1.b	The relation between TCR current and firing angle	108
4.1.c	The relation between TCR current and firing angle α	108